INDEX

S. No.	Date	Name of the Experiment	Page No.	Marks Awarded	Signature
1	21/1/2026	Verification of Kirchoff's voltage law and Kirchoff Current law.		100	
2	28/1/2026	open circuit and load characteristic of DC Shunt generator		100	
03.	04/2/2026	Staircase wiring.		99	
04.	18/02/26	Half wave and Full wave Rectifier		99	
05.	25/2/26	Zener diode as voltage Regulation		99	
06.	11/03/26	Characteristic of LVDT (characteristic variable different Transformer)		97	

Completed
11/03/26

Expt. No. 3.

Page No.

Staircase wiring

Aim

To develop and test the staircase wiring using proteus

Apparatus Required

Laptop with protues software

Theory

Staircase wiring is a common multiple way switching or two way switching connection. It in values wiring for one light with two switches. In this set up is controlled by two switches. located operate the load. from separated position above or below the stair case from inside or outside of room or two way led switch.

Procedure

Drag the required components from the process library

connect the component as

Stair Case
wiring.

Circuit diagram

2 way Switch SPDT

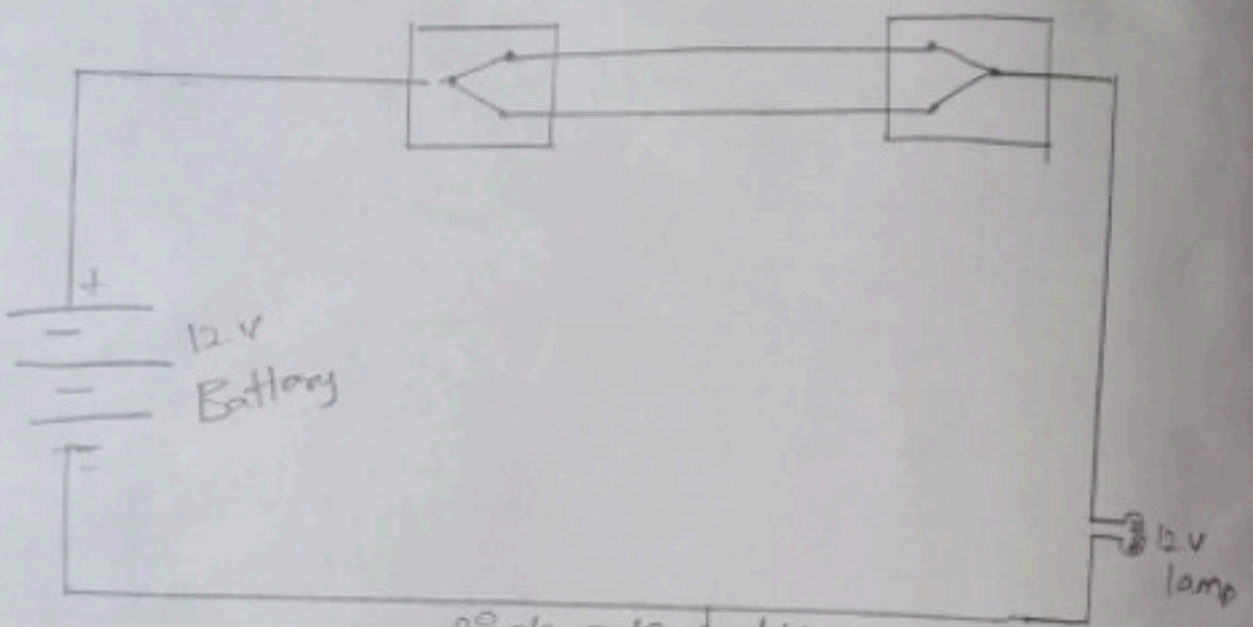

Single pole double
Throw switch

S.NO	S_1	S_2	lamp
1	on	on	on
2	on	off	off
3	off	on	off
4	off	off	on

Component	proteus	Specification
AC Supply	VSine	Application 230 V
Two way Switch	Spot	frequency 50Hz
lamp	Amimeter	230V

Expt. No. 3

Page No.

* Run the simutation and check the lamp for different switch condition

SAVEETHA
ENGINEERING COLLEGE
SAVEETHA NAGAR, THIVAL
BE THE BEST

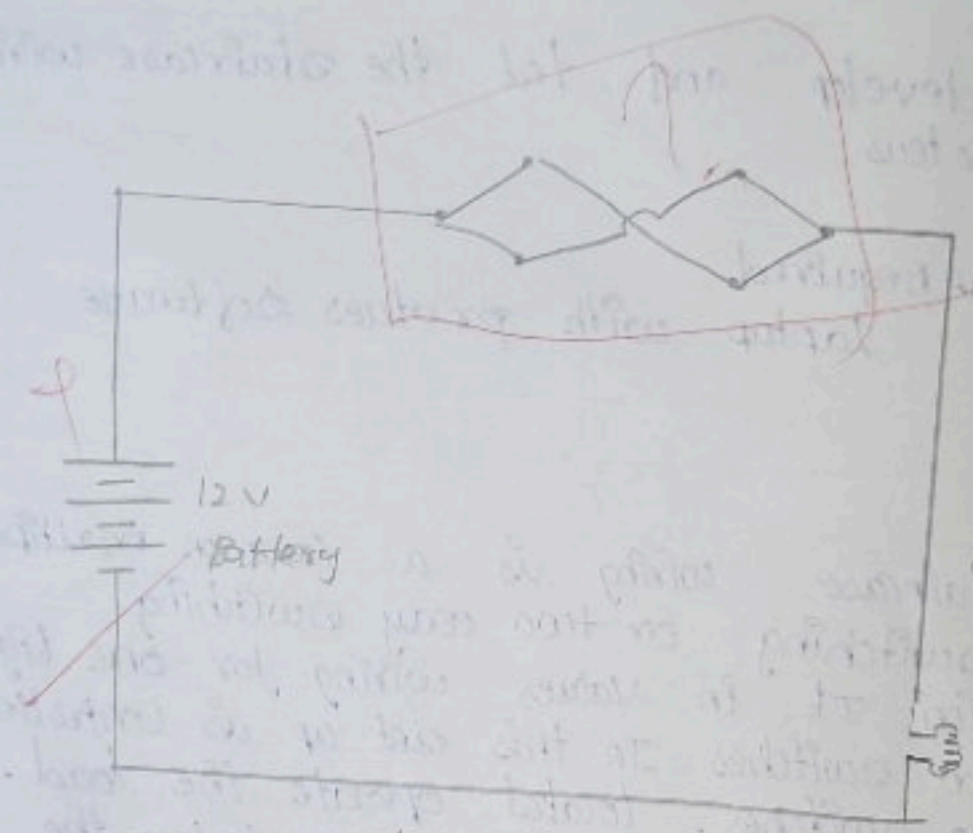

mode	S_1	S_2	Lamp
1	on	on	off
2	on	off	on
3	off	on	on
4	off	off	off

Expt. No. 3

Page No.

99

11/8/16

Result:

Thus the staircase using connection were developed and tested successfully

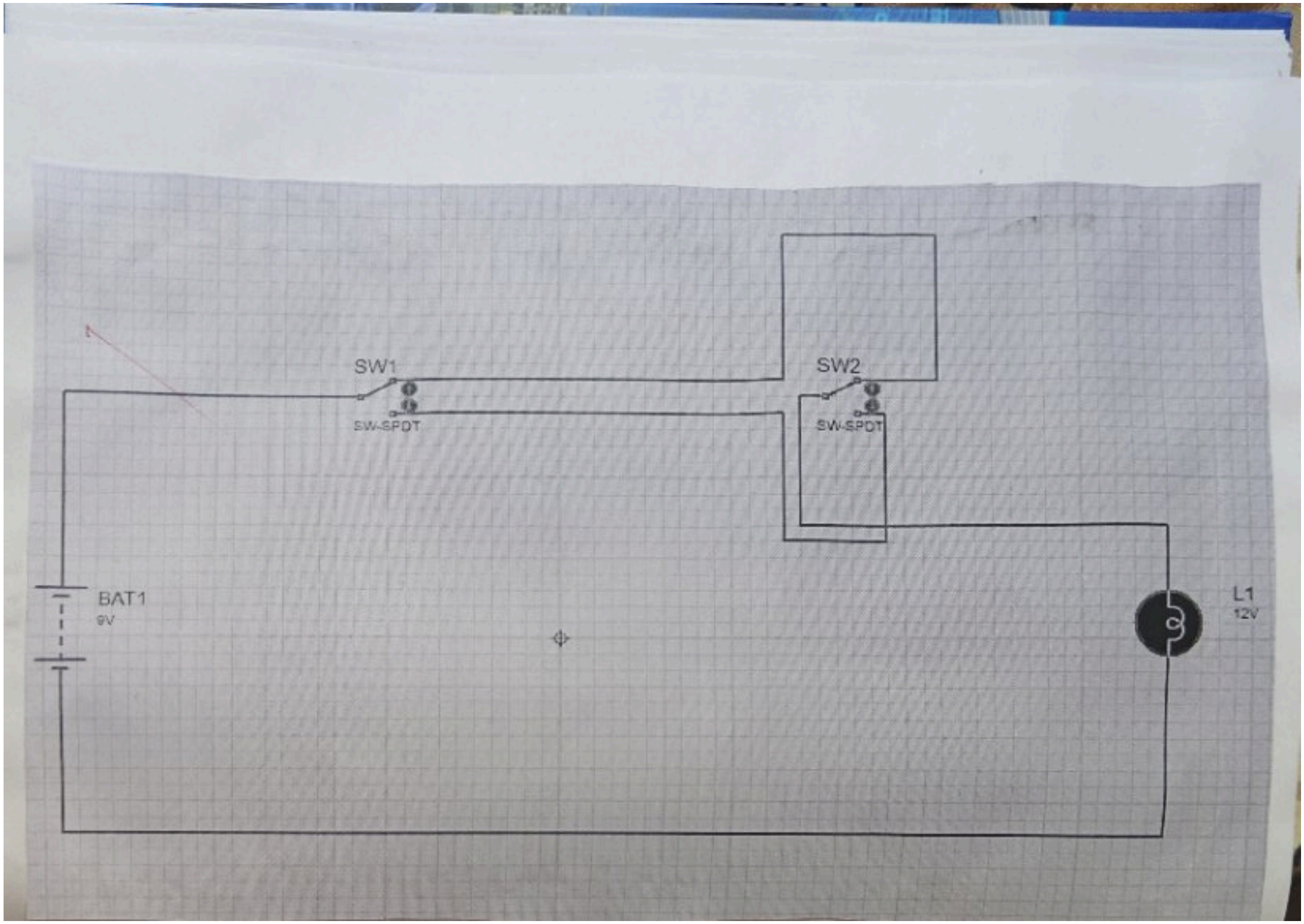
SW1
SW-SPDT
SW2
SW-SPDT
BAT1
9V
L1
12V

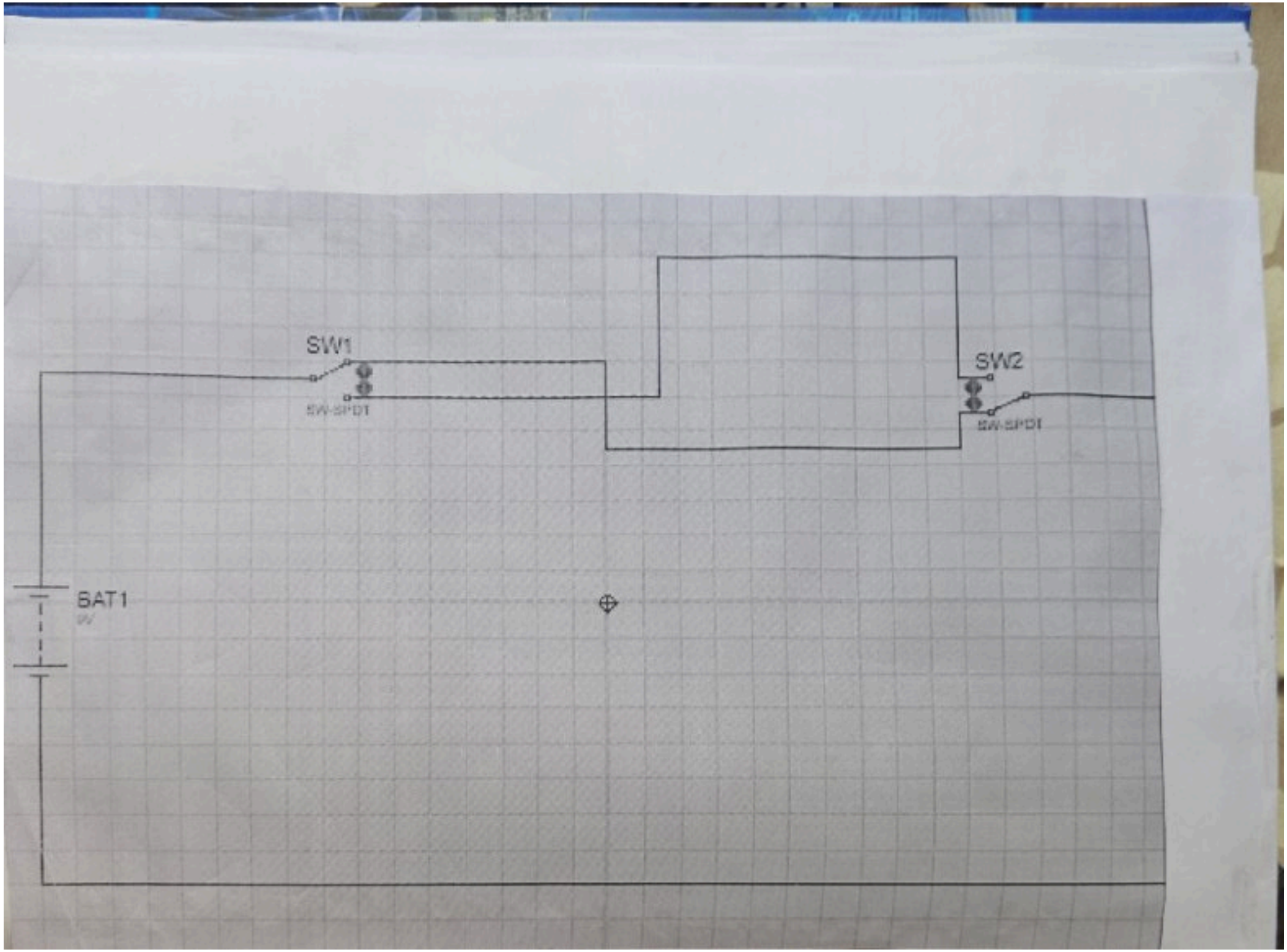
SW1
SW-SPDT
SW2
SW-SPDT
BAT1